



V Semester B.Sc. Examination, November/December 2014

(OS) (Semester Scheme) (Prior to 2013-14)

PHYSICS – V

Gravitation, Space Physics and Electronics

Time : 3 Hours

Max. Marks : 60

Instruction : Answer **five** questions from Part A, **four** questions from Part B and **five** questions from Part C.

PART – A

Answer **any five** questions. **Each** question carries **six** marks. (5×6=30)

B.M.S.C.W

1. a) State Kepler's law of planetary motion.
- b) Distinguish between inertial mass and gravitational mass. (3+3)
2. a) What is an atmospheric window ? Explain.
- b) Derive an expression for the time period of the satellite. (3+3)
3. Discuss thermodynamics of dry and moist air and hence obtain an expression for the virtual temperature. 6
4. Draw the ac equivalent circuit of CE transistor amplifier using h-parameters and hence obtain an expression for the input impedance and output impedance. 6
5. Explain with a circuit diagram how the JFET parameters can be found from the characteristics. 6
6. Explain how an op-amp can be used as Adder at the inverting mode. Derive an expression for its output. Discuss any two special cases of the connection. 6
7. Explain with a circuit diagram the action of phase shift oscillator. Write the expression for its frequency of oscillation. 6
8. a) Write a note on exclusive- OR gate.
- b) What is full adder ? Draw its block diagram using Half adder and write its truth table. (3+3)



PART - B

Solve **any four** problems. **Each** problem carries **five** marks.

(4x5=20)

9. Calculate the earth's surface potential from the given data :

Radius of the earth = 6.4×10^3 Km

Mean density = 5.5×10^3 Kg m⁻³ and

Gravitational constant = 6.66×10^{-11} Nm² Kg⁻².

10. The moon takes 27.3 days to go once round the earth in an orbit of radius 3.9×10^5 Km. Assuming the mass of the earth to be 6.3×10^{24} Kg, calculate the constant of gravitation.
11. For a zener shunt regulator if $V_Z = 10$ V, $R_S = 1$ K Ω , $R_L = 2$ K Ω and the input voltage varies from 22 to 36 V, find the maximum and minimum values of zener current.
12. The vertical gain control of a CRO is set at a deflection sensitivity 2 V Cm⁻¹. An unknown ac voltage applied to it produces a trace which is 8 cm long. Find the value of the voltage.
13. A 5 mv, 1 KHz sinusoidal signal is applied to the input of an op-amp integrator for which $R = 100$ K Ω and $C = 1$ μ F. Find the output voltage.
14. Simplify the following Boolean expression.
- a) $Y = (A + B) (A + \bar{B}) (\bar{A} + C)$
- b) $Y = ABC + A\bar{B}C + AB\bar{C}$.

PART - C

15. Answer **any five** questions. **Each** question carries **two** marks.

(5x2=10)

- a) What is a Parking orbit ? Explain.
- b) Is the Green house effect beneficial ? Explain.
- c) Does a p-n junction possess capacitance ? Explain.
- d) In what way thick film IC's are different from thin film IC's ? Explain.
- e) Can an op-amp be used as a voltage multiplier ? Explain.
- f) Does XOR gate be called an exclusively - OR ? Justify.